403 Practical Circuits

4.3.1 An unloaded potential divider

Series resistors carry the same current, so the voltage across the chosen output resistor is its fraction of total resistance times the supply voltage. Here the output is across the first resistor. Connecting a load places it in parallel with that resistor and changes the ratio; recalculate the equivalent resistance instead of reusing the unloaded result.

$$V_{\text{out}} = \frac{R_1}{R_1 + R_2}\varepsilon$$

Unloaded potential divider. Output is across R1 in the source diagram. R1, R2: Ω; ε, V_{out}: V. A connected load changes the effective resistance.

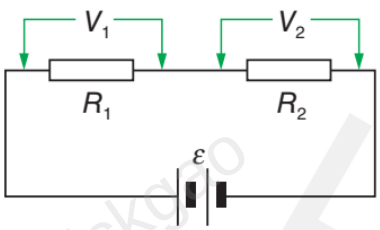


Fig 3.1d *Resistors R_1 and R_2 connected in series to a battery.*

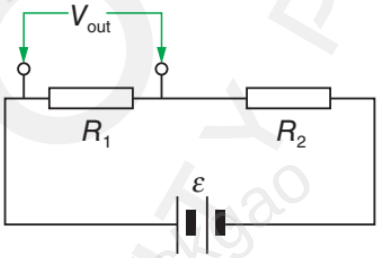


Fig 3.1e *The output voltage depends on the resistance ratio.*

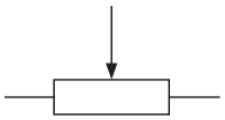


Fig 3.1f *Circuit symbol of potential divider.*

The output terminals are across R1. This is why R1, rather than R2, appears in the numerator of the displayed divider formula.

Textbook sources: 403 · PDF 4

4.3.2 Connecting an ammeter

An ammeter is connected in series so that the measured branch current passes through it. An ideal ammeter has zero resistance; a real meter disturbs the current less when its resistance is low. Connecting it across a power supply can create a near short circuit. Do not connect it like a voltmeter.

Textbook sources: 403 · PDF 11

4.3.3 Connecting a voltmeter and loading effects

A voltmeter is connected in parallel across the two points being measured. Ideally its resistance is infinite and it draws no current. A real voltmeter draws some current and can change the original voltage distribution. Higher meter resistance generally causes less disturbance, especially when measuring high-resistance circuits.

Textbook sources: 403 · PDF 12

4.3.4 Internal resistance and terminal voltage

For a discharging cell, e.m.f. equals external terminal voltage plus the drop across internal resistance. Greater current increases this internal drop and lowers terminal voltage. At zero current, terminal voltage equals e.m.f. During charging, current reverses, so the discharge subtraction relation cannot be applied without changing the sign convention.

$$\varepsilon = V + Ir$$

Discharging cell: ε: e.m.f. (V); V: terminal voltage (V); I: supplied current (A); r: internal resistance (Ω). During charging the terminal-voltage relation changes sign.

Textbook sources: 403 · PDF 19

rodrickgao